

Electric Circuits (Cont'd)

We derived eq<sup>n</sup>

$$L \frac{dI}{dt} + RI + \frac{1}{C} Q = E(t)$$

Differentiate both sides of this eq<sup>n</sup> wrt  $t$

$$L \frac{d^2 I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} I = E'(t)$$

(3)

2<sup>nd</sup> order DE for  $I(t)$

since  $\frac{dQ}{dt} = I(t)$ .

Usually we will given initial charge  $Q(0) = Q_0$  and initial

current  $I(0) = I_0$ , but to solve eq<sup>n</sup> (3) we would need  $I(0) = I_0$

and  $\frac{dI}{dt}(0) = ?$  How do find  $\frac{dI}{dt}(0)$ .

Q We will use eq<sup>n</sup> (1)

$$L \frac{dI}{dt} + RI + \frac{1}{C} Q = E(t)$$

(1)

and solve it for  $\frac{dI}{dt}$  at  $t=0$ .

known ← given as ICs

$$\left. \frac{dI}{dt} \right|_{t=0} = \frac{E(0) - RI(0) - \frac{1}{C} Q(0)}{L}$$

$$\frac{dQ}{dt} = I(t) \quad \text{or}$$

Consider again eq<sup>n</sup> (1), and recall

$$Q(t) = \int_{t_0}^t I(\tau) d\tau + Q(t_0)$$

to

Substitute  $Q(t)$  into (1) to get

$$L \frac{dI}{dt} + RI + \frac{1}{C} \left[ \int_{t_0}^t I(\tau) d\tau + \underbrace{Q(t_0)}_{\text{const}} \right] = E(t) \quad (4)$$

Eq<sup>n</sup> (4) is an integro-differential equation for  $I(t)$ .

Note If we need to find charge  $Q(t)$ , we can use eq<sup>n</sup> (2):

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = E(t), \quad Q(0) = Q_0, \quad \frac{dQ}{dt}(0) = I(0) = I_0$$

If we need to find current  $I(t)$ , we can

### Method I

Use eq<sup>y</sup> (2) to solve for  $Q(t)$  and then  $I(t) = \frac{dQ}{dt}$

### Method II

Solve eq<sup>y</sup> (3) for  $I(t)$  directly and use  $\frac{dI}{dt}$  from eq<sup>y</sup> (1), i.e.

$$L \frac{d^2 I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} I = E'(t),$$

$$I(0) = I_0 \quad \left( \begin{array}{c} I_0 \\ Q_0 \end{array} \right)$$

$$\frac{dI}{dt} \Big|_0 = \frac{E(0) - R I_0 - \frac{1}{C} Q_0}{L}$$

There is an excellent analogy with mass-spring systems:

$$m \ddot{x} + c \dot{x} + kx = 0$$

$\downarrow$   $L$        $\downarrow$   $R$        $\downarrow$   $\frac{1}{C}$

$m \leftrightarrow L$  stores energy in magnetic field

$c \leftrightarrow R$  dissipates energy

$k \leftrightarrow \frac{1}{C}$  stores energy in electric field

$$x(t) \leftrightarrow Q(t)$$

$$\dot{x}(t) \leftrightarrow I(t)$$

$\frac{1}{2} m(\dot{x})^2$  kinetic energy  $\leftrightarrow \frac{1}{2} L I^2$  magnetic energy

$\frac{1}{2} k x^2$  potential energy  $\leftrightarrow \frac{1}{2C} Q^2$  electric energy

Similar to mass-spring systems, circuits can be overdamped, critically damped or oscillatory / underdamped.

$$L \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q = 0$$

$$\left( L D^2 + R D + \frac{1}{C} \right) Q = 0$$

$$\frac{-R \pm \sqrt{R^2 - 4 \cdot L \cdot \frac{1}{C}}}{2L}$$

Everything depends on the sign of discriminant  $R^2 - 4L/C$

$R^2 > \frac{4L}{C}$  : overdamped circuit

$R^2 = \frac{4L}{C}$  : critically damped

$R^2 < \frac{4L}{C}$  : oscillatory / underdamped

Problem Find  $I(t)$  given that  $I(0) = \frac{1}{10}$  and  $Q(0) = -\frac{1}{65}$ .

$R = 2 \Omega$



$C = \frac{1}{260}$  farads

$L = \frac{1}{10}$  henries

We will use eq<sup>n</sup> (3)

$$L \frac{d^2 I}{dt^2} + R \frac{dI}{dt} + \frac{1}{C} I = 0 \quad (3)$$

$$I(0) = \frac{1}{10}, \quad \frac{dI}{dt}(0) = ? \quad \text{use 1st order coupled eqs for } I \text{ and } Q$$

$$\frac{dI}{dt}(0) = \frac{R I(0) - \frac{1}{C} Q(0)}{L} = \frac{-2 \cdot \frac{1}{10} - 260 \left(-\frac{1}{65}\right)}{\frac{1}{10}} = 38$$

$$\frac{1}{10} \frac{d^2 I}{dt^2} + 2 \frac{dI}{dt} + 260 I = 0, \quad I(0) = \frac{1}{10}, \quad \frac{dI}{dt}(0) = 38$$

We can use an operator approach, for example.

$$\left(\frac{1}{10} D^2 + 2D + 260\right) I = 0$$

$$\frac{-2 \pm \sqrt{2^2 - 4 \cdot \frac{1}{10} \cdot 260}}{2 \cdot \frac{1}{10}} = -10 \pm 50i$$

$$I(t) = C_1 e^{-10t} \cos 50t + C_2 e^{-10t} \sin 50t$$

To find  $C_1$  and  $C_2$ , we use ICs  $I(0) = \frac{1}{10}, \quad \frac{dI}{dt}(0) = 38$

We can find  $C_1 = 0.1, \quad C_2 = 0.78$

since  $I(0) = C_1$

$$\frac{dI}{dt} = C_1(-10)e^{-10t} \cos 50t - 50C_1 e^{-10t} \sin 50t - 10C_2 e^{-10t} \sin 50t + 50C_2 e^{-10t} \cos 50t$$

$$\frac{dI}{dt}(0) = -10C_1 + 50C_2 = 38 \Rightarrow C_2 = 0.78$$

" 0.1

## Chapter 7 Laplace Transforms

Ex Consider  $\int_1^3 (s+t)^3 dt$  :  $s$  is a parameter

$$\int_1^3 (s+t)^3 dt = \left. \frac{(s+t)^4}{4} \right|_{t=1}^{t=3} = \frac{(s+3)^4}{4} - \frac{(s+1)^4}{4} : \text{function of } s$$

Note  $\int_1^3 (s+t)^3 dt = \int_1^3 (s+x)^3 dx = \int_1^3 (s+p)^3 dp$

Variable of integration in definite integrals is called a "dummy variable".

Ex  $\int_1^{\infty} \frac{1}{x^2+1} dx$  : improper integral

$$\int_1^{\infty} \frac{1}{x^2+1} dx \stackrel{\text{def}}{=} \lim_{M \rightarrow \infty} \int_1^M \frac{1}{x^2+1} dx = \lim_{M \rightarrow \infty} \arctan x \Big|_{x=1}^M =$$

$$= \lim_{M \rightarrow \infty} (\arctan M - \arctan 1) = \frac{\pi}{2} - \frac{\pi}{4} = \frac{\pi}{4} : \text{finite \#} \Rightarrow \int_1^{\infty} \frac{dx}{x^2+1} \text{ converges}$$

